

# **Building a Single-cycle RISC V processor in Verilog**

## Contents

Introduction.....	3
Key features .....	3
Not conformance to specification .....	3
Control Unit signals .....	4
Immediate encoding.....	4
Branch condition codes .....	5
Destination register sources .....	5
ALU operations.....	6
ALU a and b sources .....	6
Load and store .....	6
Data access sizes .....	7
Full design (with Nexys 4 DDR IO) .....	8
Testbench.....	29
Another heading .....	35
Instruction Set Architecture.....	36
References .....	41

# Introduction

## Key features


The ALU will process two inputs – a and b. Input a can be either the rs1 value or the program counter. Input b can be either the rs2 value or the extended immediate value.

The ALU is used for branch calculations.

There is a separate adder to add 4 to the program counter for the next instruction.

Branches are taken if the branch condition unit calculates a true value. It can compare the rs1 and rs2 values to determine whether to branch. The nature of the comparison is derived by the control unit.

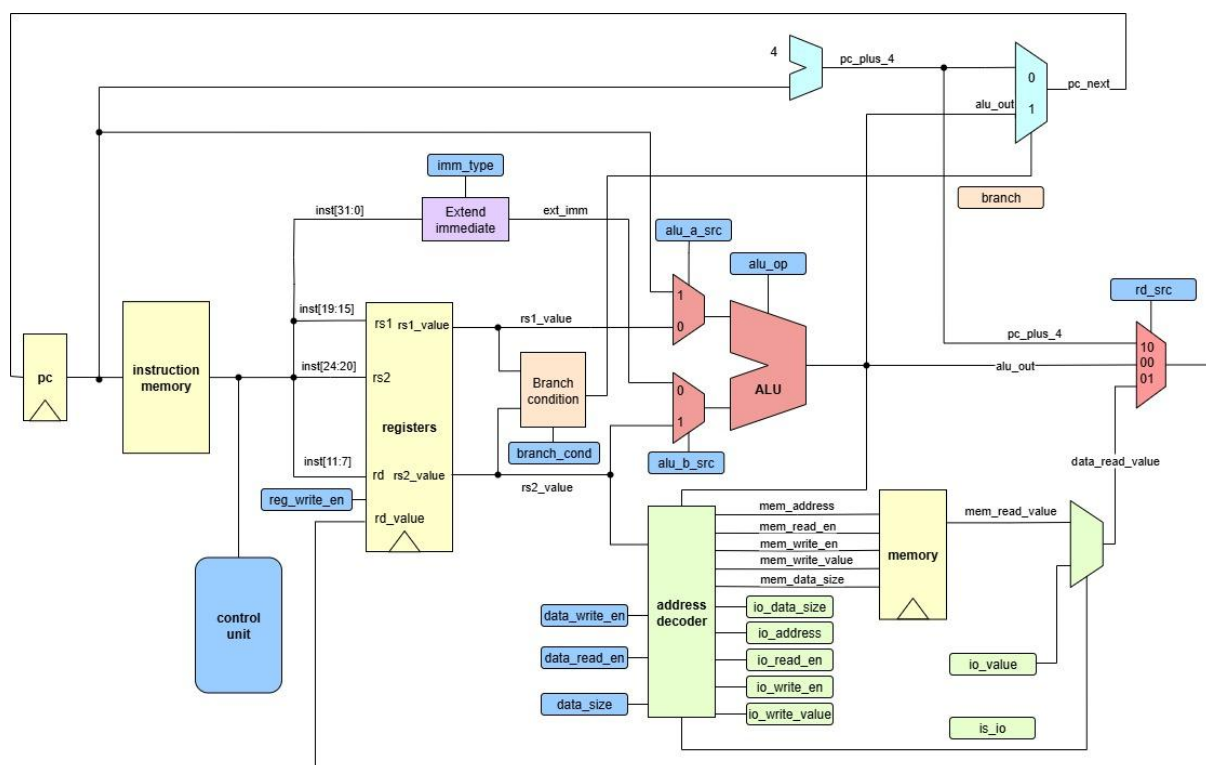The clocked components are the memory, the register file and the program counter



## Not conformance to specification

Misaligned memory loads and stores will not be handled according to the specification – the memory address will be truncated to the lower aligned address. For example, a word access to byte 7 will be truncated down to byte 4.

## Control Unit signals

### Signal definitions


Signal	Definition
imm_type	Type of immediate (B, I, J, S, U, R)
alu_a_src	a input to ALU (pc, rs1)
alu_b_src	b input to ALU (imm, rs2)
alu_op	Function for ALU to execute
rd_src	Source for rd register (data, pc + 4, alu output)
reg_write_en	Write to rd register
data_read_en	Enable read from data bus
data_write_en	Enable write to data bus
data_size	Data access size of data (byte, half-word, word)
branch_cond	Branch comparison to perform (==, !=, <, >=)

### Signals for each opcode

Instruction	opcode	Control Unit signals									
		imm_type	alu_a_src	alu_b_src	rd_src	reg_write_en	data_read_en	data_write_en	data_size	alu_op	branch_cond
arithmetic reg	011_0011	0	0	0	00	1	0	0	000	see table	010
arithmetic imm	001_0011	1	0	1	00	1	0	0	000	see table	010
load	000_0011	1	0	1	01	1	1	0	see table	0000	010
store	010_0011	2	0	1	00	0	0	1	see table	0000	010
branch	110_0011	3	1	1	00	0	0	0	000	0000	see table
jal	110_1111	4	1	1	00	0	0	0	000	0000	011
jalr	110_0111	1	0	1	10	1	0	0	000	0000	011
lui	011_0111	5	0	1	00	1	0	0	000	1001	010
auipc	001_0111	5	1	1	00	1	0	0	000	0000	010

### Immediate encoding

instruction	opcode	imm_type	immediate
arithmetic reg	011_0011	0	R
arithmetic imm	001_0011	1	I
load	000_0011	1	I
store	010_0011	2	S
branch	110_0011	3	B
jal	110_1111	4	J
jalr	110_0111	1	I
lui	011_0111	5	U
auipc	001_0111	5	U

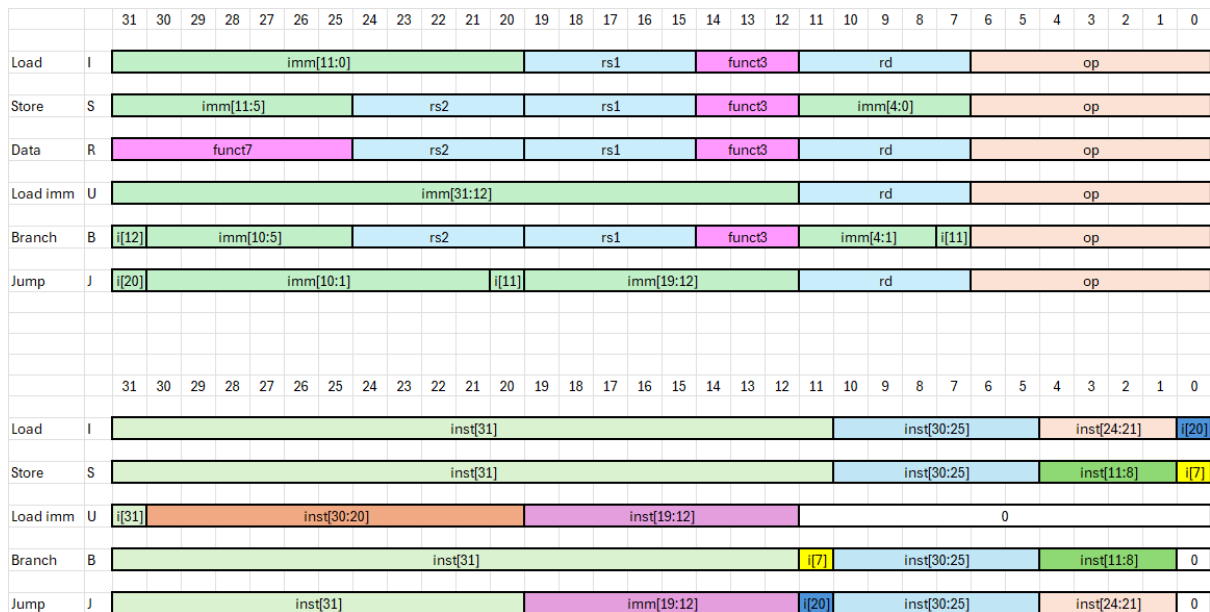

## Branch condition codes

These specify the comparisons for the branch unit to make

For instructions that do not branch this is set to ‘no branch’

For jal and jalr which always branch this is set to ‘always branch’

Fortunately in the ISA there were two values spare to use for these.

Value	Description
000	a == b
001	a != b
010	no branch
011	always branch
100	signed(a) < signed(b)
101	signed(a) >= signed(b)
110	a < b
111	a >= b

## Destination register sources

The rd register can store the output of the ALU, the value read from memory or IO, or the location of the next instruction (pc+4)

Value	Description
00	alu_out
01	data_read_value
10	pc + 4
11	

## ALU operations

These are the operations the ALU can perform.

The final one will pass the b input to the output (immediate), required for the **lui** instruction.

Apart from the arithmetic instructions, and lui, alu\_op will be 0000 (add)

opcode	funct3	funct7[5]	Operation	Function	ALU Op
0?1_0011	000	0	add	alu_out = a + b	0000
0?1_0011	000	1	sub	alu_out = a - b	1000
0?1_0011	001	0	sll	alu_out = a << b[4:0]	0001
0?1_0011	010	0	slt	alu_out = a < signed(b) ? 1 : 0	0010
0?1_0011	011	0	sltu	alu_out = a < unsigned(b) ? 1 : 0	0011
0?1_0011	100	0	xor	alu_out = a ^ b	0100
0?1_0011	101	0	srl	alu_out = a >> b[4:0]	0101
0?1_0011	101	1	sra	alu_out = a >>> b[4:0]	1101
0?1_0011	110	0	or	alu_out = a   b	0110
0?1_0011	111	0	and	alu_out = a & b	0111
				alu_out = b	1001

The arithmetic instruction opcodes are 001\_0011 for immediate (addi) and 011\_0011 for register (add)

For the arithmetic instructions, the input values of a is rs1 and b is either rs2 or the immediate

Value	alu_a	alu_b
001_0011	rs1	immediate
011_0011	rs1	rs2

## ALU a and b sources

The a source can be rs1 or pc

The b source can be rs2 or the immediate

Value	Source
0	rs1
1	pc

Value	Source
0	rs2
1	ext_imm

## Load and store

Xxxxx

## Data access sizes

Memory and IO access can be of various data sizes: byte, half-word or word. Data reads can be extended as signed or unsigned.

Value	Description
000	byte
001	half-word
010	word
011	
100	unsigned byte
101	unsigned half-word
110	
111	

## Full design (with Nexys 4 DDR IO)

Verilog file: top.v

```
`timescale 1ns / 1ps

module top(
    input    CLK100MHZ,
    input    [15:0] SW,
    input    [4:0]  BTN,
    output reg [15:0] LED
);

wire [31:0] io_address;
wire [31:0] io_write_value;
reg  [31:0] io_read_value;
wire        io_write_en;
wire        io_read_en;
wire [2:0]  io_data_size;

Risc32 risc(
    .clk(CLK100MHZ),
    .io_address(io_address),
    .io_write_value(io_write_value),
    .io_read_value(io_read_value),
    .io_write_en(io_write_en),
    .io_read_en(io_read_en),
    .io_data_size(io_data_size)
);

always @(*)
begin
    case (io_address[1:0])
        2'b01: io_read_value <= {16'b0, SW};
        2'b10: io_read_value <= {27'b0, BTN};
        default: io_read_value <= 32'b0;
    endcase
end

always @(posedge CLK100MHZ)
begin
    if (io_write_en && io_address[2]) // bit 2 is set in the write address
        LED <= io_write_value[15:0];
    end
endmodule
```



## Verilog file: processor.v

```
module Risc32(
    input      clk,
    output [31:0] io_address,
    output [31:0] io_write_value,
    input  [31:0] io_read_value,
    output      io_write_en,
    output      io_read_en,
    output [2:0] io_data_size
);

// Control unit signals
wire [2:0] cu_branch_cond;
wire      cu_data_read_en;
wire      cu_data_write_en;
wire [2:0] cu_data_size;
wire [1:0] cu_rd_src;
wire      cu_reg_write_en;
wire      cu_alu_b_src;
wire      cu_alu_a_src;
wire [3:0] cu_alu_op;
wire [2:0] cu_imm_type;

// Opcode from datapath to control unit
wire [6:0] dp_opcode;
wire [6:0] dp_funct7;
wire [2:0] dp_funct3;

// Datapath
DatapathUnit datapath
(
    .clk(clk),
    .imm_type(cu_imm_type),
    .branch_cond(cu_branch_cond),
    .data_read_en(cu_data_read_en),
    .data_write_en(cu_data_write_en),
    .alu_b_src(cu_alu_b_src),
    .alu_a_src(cu_alu_a_src),
    .rd_src(cu_rd_src),
    .reg_write_en(cu_reg_write_en),
    .alu_op(cu_alu_op),
    .data_size(cu_data_size),
    .opcode(dp_opcode),
    .funct7(dp_funct7),
    .funct3(dp_funct3),
    .io_address(io_address),
    .io_write_value(io_write_value),
    .io_read_value(io_read_value),
    .io_write_en(io_write_en),
    .io_read_en(io_read_en),
    .io_data_size(io_data_size)
);

// control unit
ControlUnit control
(
    .opcode(dp_opcode),
    .funct7(dp_funct7),
    .funct3(dp_funct3),
    .imm_type(cu_imm_type),
    .rd_src(cu_rd_src),
    .alu_op(cu_alu_op),
    .branch_cond(cu_branch_cond),
```

```
.data_read_en(cu_data_read_en),  
.data_write_en(cu_data_write_en),  
.data_size(cu_data_size),  
.alu_b_src(cu_alu_b_src),  
.alu_a_src(cu_alu_a_src),  
.reg_write_en(cu_reg_write_en)  
);
```

## Verilog file: control-unit.v

```

module ControlUnit(
    input      [6:0] opcode,
    input      [6:0] funct7,
    input      [2:0] funct3,
    output reg [2:0] imm_type,
    output reg [3:0] alu_op,
    output reg [2:0] branch_cond,
    output reg      data_read_en,
    output reg      data_write_en,
    output reg [2:0] data_size,
    output reg [1:0] rd_src,
    output reg      reg_write_en,
    output reg      alu_b_src,
    output reg      alu_a_src
);

always @(*)
begin
    case(opcode)
        7'b001_0011: // arithmetic with immediate
                        // only need funct7 when funct 3 is 3'b101 (srli / srai)
                        // could also include for 3'b001 (slli)
            begin
                imm_type      = 3'd1;    // type I
                alu_a_src      = 1'b0;    // rs1
                alu_b_src      = 1'b1;    // imm
                rd_src         = 2'b00;   // data from alu
                reg_write_en   = 1'b1;    // write to rd
                data_read_en   = 1'b0;    // no read from memory
                data_write_en  = 1'b0;    // no write to memory
                branch_cond    = 3'b010;  // no branch
                alu_op         = {funct3 == 3'b101 ? funct7[5] : 0, funct3}; // alu_op has
                data_size      = 3'b000;
            end
        7'b011_0011: // arithmetic with registers
                        // funct7 encoded for all alu_op operations
                        // even if only used for 3'b101 and 3'b000 (add/sub and srl/sra)
            begin
                imm_type      = 3'd0;    // type R
                alu_a_src      = 1'b0;    // rs1
                alu_b_src      = 1'b0;    // rs2
                rd_src         = 2'b00;   // data from alu
                reg_write_en   = 1'b1;    // write to rd
                data_read_en   = 1'b0;    // no read from memory
                data_write_en  = 1'b0;    // no write to memory
                branch_cond    = 3'b010;  // no branch
                alu_op         = {funct7[5], funct3}; // alu_op has been encoded to match this
                data_size      = 3'b000;
            end
        7'b110_0111: // jalr
            begin
                imm_type      = 3'd1;    // type I
                alu_a_src      = 1'b0;    // rs1
                alu_b_src      = 1'b1;    // ext_imm
                rd_src         = 2'b10;   // pc + 4
                reg_write_en   = 1'b1;    // write to rd
                data_read_en   = 1'b0;    // no read from memory
                data_write_en  = 1'b0;    // no write to memory
                branch_cond    = 3'b011;  // branch always
                alu_op         = 4'b0000; // add
                data_size      = 3'b000;
            end
    endcase
end

```

```

end
7'b110_1111: // jal
begin
    imm_type      = 3'd4;    // type J
    alu_a_src     = 1'b1;    // pc_current
    alu_b_src     = 1'b1;    // ext_imm
    rd_src        = 2'b10;   // pc + 4
    reg_write_en  = 1'b1;    // write to rd
    data_read_en  = 1'b0;    // no read from memory
    data_write_en = 1'b0;    // no write to memory
    branch_cond   = 3'b011;  // branch always
    alu_op        = 4'b0000; // add
    data_size     = 3'b000;
end
7'b010_0011: // store
begin
    imm_type      = 3'd2;    // type S
    alu_a_src     = 1'b0;    // rs1
    alu_b_src     = 1'b1;    // ext_imm
    rd_src        = 2'b00;   // data from alu
    reg_write_en  = 1'b0;    // no write to rd
    data_read_en  = 1'b0;    // no read from memory
    data_write_en = 1'b1;    // no write to memory
    branch_cond   = 3'b010;  // no branch
    alu_op        = 4'b0000; // add
    data_size     = funct3;
end
7'b000_0011: // load
begin
    imm_type      = 3'd1;    // type I
    alu_a_src     = 1'b0;    // rs1
    alu_b_src     = 1'b1;    // ext_imm
    rd_src        = 2'b01;   // data from memory
    reg_write_en  = 1'b1;    // write to rd
    data_read_en  = 1'b1;    // read from memory
    data_write_en = 1'b0;    // no write to memory
    branch_cond   = 3'b010;  // no branch
    alu_op        = 4'b0000; // add
    data_size     = funct3;
end
7'b011_0111: // lui
begin
    imm_type      = 3'd5;    // type U
    alu_a_src     = 1'b0;    // rs1
    alu_b_src     = 1'b1;    // imm
    rd_src        = 2'b00;   // data from alu
    reg_write_en  = 1'b1;    // write to rd
    data_read_en  = 1'b0;    // no read from memory
    data_write_en = 1'b0;    // no write to memory
    branch_cond   = 3'b010;  // no branch
    alu_op        = 4'b1001; // pass through alu_b
    data_size     = 3'b000;
end
7'b001_0111: // auipc
begin
    imm_type      = 3'd5;    // type U
    alu_a_src     = 1'b1;    // pc
    alu_b_src     = 1'b1;    // imm
    rd_src        = 2'b00;   // data from alu
    reg_write_en  = 1'b1;    // write to rd
    data_read_en  = 1'b0;    // no read from memory
    data_write_en = 1'b0;    // no write to memory
    branch_cond   = 3'b010;  // no branch
    alu_op        = 4'b0000; // add
    data_size     = 3'b000;
end

```

```

7'b110_0011: // branch
begin
    imm_type      = 3'd3;    // type B
    alu_a_src     = 1'b1;    // pc_current
    alu_b_src     = 1'b1;    // ext_imm
    rd_src        = 2'b00;   // data from alu
    reg_write_en  = 1'b0;    // no write to rd
    data_read_en  = 1'b0;    // no read from memory
    data_write_en = 1'b0;    // no write to memory
    branch_cond   = funct3;  // branch condition is encoded to match funct3
    alu_op        = 4'b0000; // add
    data_size     = 3'b000;
end
default: // ADD
begin
    imm_type      = 3'd0;    // type R
    alu_a_src     = 1'b0;
    alu_b_src     = 1'b0;
    rd_src        = 2'b00;
    reg_write_en  = 1'b1;
    data_read_en  = 1'b0;
    data_write_en = 1'b0;
    branch_cond   = 3'b010;  // no branch
    alu_op        = 4'b0000;
    data_size     = 3'b000;
end
endcase

```

## Verilog file: datapath.v

```
module DatapathUnit(
    input      clk,
    input  [2:0] imm_type,
    input  [2:0] branch_cond,
    input      data_read_en,
    input      data_write_en,
    input      reg_write_en,
    input  [2:0] data_size,
    input  [1:0] rd_src,
    input      alu_b_src,
    input      alu_a_src,
    input  [3:0] alu_op,
    output [6:0] opcode,
    output [6:0] funct7,
    output [2:0] funct3,

    output [31:0] io_address,
    output [31:0] io_write_value,
    input  [31:0] io_read_value,
    output      io_write_en,
    output      io_read_en,
    output [2:0] io_data_size
);

    reg  [31:0] pc_current;
    wire [31:0] pc_next;
    wire [31:0] pc_plus_4;

    wire      branch_control;

    wire [4:0] rd;
    wire [31:0] rd_value;
    wire [4:0] rs1;
    wire [31:0] rs1_value;
    wire [4:0] rs2;
    wire [31:0] rs2_value;

    wire [31:0] instr;
    reg  [31:0] ext_imm;
    wire [31:0] alu_b_in;
    wire [31:0] alu_a_in;
    wire [31:0] alu_out;

    wire [31:0] data_read_value;

    wire      is_io;
    wire [31:0] mem_address;
    wire [31:0] mem_read_value;
    wire [31:0] mem_write_value;
    wire      mem_read_en;
    wire      mem_write_en;
    wire [2:0] mem_data_size;

    // Note that io_address is part of the interface
    // Note that io_read_value is part of the interface
    // Note that io_write_value is part of the interface
    // Note that io_read_en is part of the interface
    // Not that io_write_en are part of the interface

    ////
    //// Program counter
    ////
```

```

initial begin
    pc_current <= 32'd0;
end

// Update to pc_next on rising clock
// Note - the last bit is set to 0 just in case JALR had set it (the only case where
it could be non-zero)
always @(posedge clk)
begin
    pc_current <= {pc_next[31:1], 1'b0};    // last bit set to 0(for JALR)
end

assign pc_plus_4 = pc_current + 32'd4;

////
//// Instruction memory
////

InstructionMemory im
(
    .pc(pc_current),
    .instruction(instr)
);

assign opcode = instr[6:0];
assign funct3 = instr[14:12];
assign funct7 = instr[31:25];

assign rs1    = instr[19:15];
assign rs2    = instr[24:20];
assign rd     = instr[11:7];

////
//// Registers
////

// Write back the destination register value - either ALU output
// MEM_READ_MUX

Mux2_32 mem_read_mux(
    .sel(is_io),
    .out(data_read_value),
    .in0(mem_read_value),
    .in1(io_read_value)
);

// RD_VALUE_MUX

Mux4_32 read_value_mux(
    .sel(rd_src),
    .out(rd_value),
    .in0(alu_out),
    .in1(data_read_value),
    .in2(pc_plus_4),
    .in3(alu_out)           // should never be selected
);

// Register allocations

RegisterUnit reg_file (
    .clk(clk),
    .reg_write_en(reg_write_en),
    .rd(rd),
    .rd_value(rd_value),
    .rs1(rs1),
    .rs1_value(rs1_value),

```

```

        .rs2(rs2),
        .rs2_value(rs2_value)
    );

    ///
    /// ext_imm
    ///

    always @(*)
    case (imm_type)
        3'd1: ext_imm = { {21{instr[31]}}, instr[30:25], instr[24:21], instr[20] };
    // I type (load)
        3'd2: ext_imm = { {21{instr[31]}}, instr[30:25], instr[11:8], instr[7] };
    // S type (store)
        3'd3: ext_imm = { {20{instr[31]}}, instr[7], instr[30:25], instr[11:8],
1'b0}; // B type - effectively making ext_imm the full offset to branch
        3'd4: ext_imm = { {12{instr[31]}}, instr[19:12], instr[20], instr[30:21],
1'b0}; // J type - effectively making ext_imm the full offset to branch
        3'd5: ext_imm = { instr[31], instr[30:20], instr[19:12], 12'b0 };
    // U type
        default: ext_imm = { {21{instr[31]}}, instr[30:25], instr[24:21], instr[20] };
    // includes R type, does not matter what it is
    endcase

    // ALU_IN_MUX
    // determine input for alu - either the rs2 value or the extended immediate value

    Mux2_32 alu_a_mux (
        .sel(alu_a_src),
        .out(alu_a_in),
        .in0(rs1_value),
        .in1(pc_current)
    );

    Mux2_32 alu_b_mux (
        .sel(alu_b_src),
        .out(alu_b_in),
        .in0(rs2_value),
        .in1(ext_imm)
    );

    // set up the ALU with rs1 and alu_in as inputs - exposes zero flag for branching
    ALU alu_unit (
        .a(alu_a_in),
        .b(alu_b_in),
        .alu_control(alu_op),
        .result(alu_out)
    );

    ///
    /// Branch control
    ///

    // BRANCH_MUX
    // The PC increments by 4
    // If a branch is needed, branch_control is true, and the destination is set a PC +
ext_imm
    // If a jump is needed, the jump destination is calculated
    // Then pc_next set to the correct value - PC + 4, branch destination or jump
destination

    // Branch comparator - do the comparsion based on branch_cond and set branch_control
to 1 if a branch is needed
    BranchComp br_comp (
        .a(rs1_value),

```



```

        .b(rs2_value),
        .branch_cond(branch_cond),
        .branch(branch_control)
    );

    // Then select which is the new pc
    Mux2_32 branch_calc (
        .sel(branch_control),
        .out(pc_next),
        .in0(pc_plus_4),
        .in1(alu_out)
    );

    ////
    //// Address decoder
    ////

    AddressDecoder ad (
        .data_address(alu_out),
        .data_read_en(data_read_en),
        .data_write_en(data_write_en),
        .data_write_value(rs2_value),
        .data_size(data_size),
        .mem_address(mem_address),
        .mem_read_en(mem_read_en),
        .mem_write_en(mem_write_en),
        .mem_write_value(mem_write_value),
        .mem_data_size(mem_data_size),
        .io_address(io_address),
        .io_read_en(io_read_en),
        .io_write_en(io_write_en),
        .io_write_value(io_write_value),
        .io_data_size(io_data_size),
        .is_io(is_io)
    );

    // Data memory

    DataMemory dm
    (
        .clk(clk),
        .mem_access_addr(mem_address),
        .mem_in(mem_write_value),
        .mem_write_en(mem_write_en),
        .mem_read_en(mem_read_en),
        .mem_out(mem_read_value),
        .mem_data_size(mem_data_size)
    );

    // IO
    // io_address, io_read_en and io_write_en set above
    // io_read_value is an input set in the other side of the IO interface
    // so only io_write_value to assign here
    ///assign io_write_value = rs2_value;

endmodule

```

## Verilog file: settings.vh

```
`ifndef SETTINGS_H
`define SETTINGS_H

// PROGRAM CHOICE
// There are two base programs, risc_io_prog and test_risc_prog
// risc_io_prog reads the switches and buttons (on a Nexys 4 DDR) and reflects that on
the LEDs
// test_risc_prog runs a basic RISC V program to check the results
// IO_DEMO selects risc_io_prog else test_risc_prog is used
`define IO_DEMO

// MEMORY SETTINGS
// Memory can be either 4 banks each of width one byte, or one array of 32 bit words
// BANKED_MEM selects the 4 banks

//`define BANKED_MEM

// Select the size (in bytes) of data memory and instruction memory
`define data_bytes      128
`define instr_bytes     128

// TESTBENCH SETTINGS

// PROG_BASIC will run the program in instruction memory for 200 steps - works for any
program
// PROG_STEPPED will run each line and check the output (requires test_risc_prog so best
to use with IO_DEMO undefined)
// PROG_INDIV will run specific commands and is not dependent on data memory or
instruction memory being initialised

//`define PROG_BASIC

//`define PROG_STEPPED
//`undef IO_DEMO

`define PROG_INDIV

`endif
```

### Verilog file: instruction\_memory.v

```
`include "settings.vh"

`define instr_addr_bits      $clog2(`instr_bytes)

module InstructionMemory(
    input  [31:0] pc,
    output [31:0] instruction
);

    // create the memory
    reg [31:0] memory [`instr_addr_bits - 1:0];

    // memory access will wrap at the limit of the number of words, and is word aligned so
    // we ignore the lower two bits
    wire [`instr_addr_bits - 1 : 0] rom_addr = pc[`instr_addr_bits + 1 : 2];

    initial
        begin
            `ifdef IO_DEMO
                $readmemb("risc_io_prog.mem", memory);
            `else
                $readmemb("risc_io_prog.mem", memory);
            `endif
        end

    assign instruction = memory[rom_addr];
endmodule
```

## Verilog file: data\_memory.v

```
`include "settings.vh"

`define data_addr_bits    $clog2(`data_bytes)
`define bank_data_bits    (`data_addr_bits - 2)
`define bank_data_bytes   (`data_bytes >> 2)

module DataMemory(
    input clk,
    // address input, shared by read and write port
    input [31:0] mem_access_addr,
    input [31:0] mem_in,
    input        mem_write_en,
    input        mem_read_en,
    input [2:0]   mem_data_size,
    output reg [31:0] mem_out
);

`ifdef BANKED_MEM
    // *****
    // ** MEMORY IS 4 BANKS EACH ONE BYTE WIDE **
    // *****

    // four banks, A is msb and D is lsb

    reg [7:0] memA [`bank_data_bytes - 1:0];
    reg [7:0] memB [`bank_data_bytes - 1:0];
    reg [7:0] memC [`bank_data_bytes - 1:0];
    reg [7:0] memD [`bank_data_bytes - 1:0];

    // this needs to split the address range into highest `data_addr_bits-3 and bottom 2
    // bits
    wire [`data_addr_bits - 3:0] word_addr; // don't need the bottom two bits - that is
    // the bank
    wire [1:0] bank_sel;

    // this needs to span the entire address range of [`data_addr_bits-1 : 0]
    // and will also wrap addresses outside of this range into the range
    assign word_addr = mem_access_addr[`data_addr_bits - 1 : 2];
    assign bank_sel  = mem_access_addr[1:0];

    initial
    begin
        `ifdef IO_DEMO
            $readmemb("risc_io_ramA.mem", memA);
            $readmemb("risc_io_ramB.mem", memB);
            $readmemb("risc_io_ramC.mem", memC);
            $readmemb("risc_io_ramD.mem", memD);
        `else
            $readmemb("test_risc_ramA.mem", memA);
            $readmemb("test_risc_ramB.mem", memB);
            $readmemb("test_risc_ramC.mem", memC);
            $readmemb("test_risc_ramD.mem", memD);
        `endif
    end

    always @(posedge clk) begin
        if (mem_write_en)
            begin
                case (mem_data_size)
                    3'b000:
                        case (bank_sel)
                            2'b00: memD[word_addr] <= mem_in[7:0];

```

```

        2'b01:    memC[word_addr] <= mem_in[7:0];
        2'b10:    memB[word_addr] <= mem_in[7:0];
        2'b11:    memA[word_addr] <= mem_in[7:0];
    endcase
3'b001:
    case (bank_sel)
        2'b00, 2'b01:    // only allow half-word aligned writes - ignore the lower
bit
        begin
            memD[word_addr] <= mem_in[7:0];
            memC[word_addr] <= mem_in[15:8];
        end
        2'b10, 2'b11:
        begin
            memB[word_addr] <= mem_in[7:0];
            memA[word_addr] <= mem_in[15:8];
        end
    endcase
    default: // really 3'b010
    begin
        memD[word_addr] <= mem_in[7:0];
        memC[word_addr] <= mem_in[15:8];
        memB[word_addr] <= mem_in[23:16];
        memA[word_addr] <= mem_in[31:24];
    end
    endcase
end
end

always @(*) begin
    if (mem_read_en)
        case (mem_data_size)
            3'b000:    // lb
            case (bank_sel)
                2'b00:    mem_out = { {24{ memD[word_addr][7] }}, memD[word_addr]};
                2'b01:    mem_out = { {24{ memC[word_addr][7] }}, memC[word_addr]};
                2'b10:    mem_out = { {24{ memB[word_addr][7] }}, memB[word_addr]};
                2'b11:    mem_out = { {24{ memA[word_addr][7] }}, memA[word_addr]};
            endcase
            3'b100:    // lbu
            case (bank_sel)
                2'b00:    mem_out = { 24'b0, memD[word_addr]};
                2'b01:    mem_out = { 24'b0, memC[word_addr]};
                2'b10:    mem_out = { 24'b0, memB[word_addr]};
                2'b11:    mem_out = { 24'b0, memA[word_addr]};
            endcase
            3'b001:    // lh
            case (bank_sel)
                2'b00, 2'b01:
                mem_out = { {16{ memC[word_addr][7]}}, memC[word_addr], memD[word_addr]};
                2'b10, 2'b11:
                mem_out = { {16{ memA[word_addr][7]}}, memA[word_addr], memB[word_addr]};
            endcase
            3'b101:
            case (bank_sel) // lhu
                2'b00, 2'b01: mem_out = { 16'b0, memC[word_addr], memD[word_addr]};
                2'b10, 2'b11: mem_out = { 16'b0, memA[word_addr], memB[word_addr]};
            endcase
            default:    // lw        really 3010
            mem_out = {memA[word_addr], memB[word_addr], memC[word_addr],
memD[word_addr]};
        endcase
    else
        mem_out = 32'd0;
    end
end

```

```

`else
// *****
// ** MEMORY IS ONE BANK 32 BITS WIDE **
// *****

reg [31:0] mem [`data_bytes - 1:0];

// this needs to split the address range into highest `data_addr_bits-3 and bottom 2
bits
wire [`data_addr_bits - 3:0] word_addr; // don't need the bottom two bits - that is
the bank
wire [1:0] byte_sel;

// this needs to span the entire address range of [`data_addr_bits-1 : 0]
// and will also wrap addresses outside of this range into the range
assign word_addr = mem_access_addr[`data_addr_bits - 1 : 2];
assign byte_sel = mem_access_addr[1:0];

initial
begin
`ifdef IO_DEMO
    $readmemb("risc_io_mem_word.mem", mem);
`else
    $readmemb("test_risc_mem_word.mem", mem);
`endif
end

always @(posedge clk) begin
    if (mem_write_en)
        begin
            case (mem_data_size)
                3'b000:
                    case (byte_sel)
                        2'b00: mem[word_addr][7:0] <= mem_in[7:0];
                        2'b01: mem[word_addr][15:8] <= mem_in[7:0];
                        2'b10: mem[word_addr][23:16] <= mem_in[7:0];
                        2'b11: mem[word_addr][31:24] <= mem_in[7:0];
                    endcase
                3'b001:
                    case (byte_sel)
                        2'b00, 2'b01: // only allow half-word aligned writes - ignore the lower
bit
                            begin
                                mem[word_addr][15:0] <= mem_in[15:0];
                            end
                        2'b10, 2'b11:
                            begin
                                mem[word_addr][31:16] <= mem_in[15:0];
                            end
                    endcase
                default: // really 3'b010
                    begin
                        mem[word_addr] <= mem_in;
                    end
            endcase
        end
    end

always @(*) begin
    if (mem_read_en)
        case (mem_data_size)
            3'b000: // 1b
                case (byte_sel)
                    2'b00:

```

```

        mem_out = { {24{ mem[word_addr][7] }}, mem[word_addr][7:0]};
    2'b01:
        mem_out = { {24{ mem[word_addr][15] }}, mem[word_addr][15:8]};
    2'b10:
        mem_out = { {24{ mem[word_addr][23] }}, mem[word_addr][23:16]};
    2'b11:
        mem_out = { {24{ mem[word_addr][31] }}, mem[word_addr][31:24]};
    endcase
3'b100:      // lbu
    case (byte_sel)
        2'b00:      mem_out = { 24'b0, mem[word_addr][7:0]};
        2'b01:      mem_out = { 24'b0, mem[word_addr][15:8]};
        2'b10:      mem_out = { 24'b0, mem[word_addr][23:16]};
        2'b11:      mem_out = { 24'b0, mem[word_addr][31:24]};
    endcase
3'b001:      // lh
    case (byte_sel)
        2'b00, 2'b01: mem_out = { {16{ mem[word_addr][15] }}, mem[word_addr][15:0]};
        2'b10, 2'b11: mem_out = { {16{ mem[word_addr][31] }}, mem[word_addr][31:16]};
    endcase
3'b101:
    case (byte_sel) // lhu
        2'b00, 2'b01: mem_out = { 16'b0, mem[word_addr][15:0]};
        2'b10, 2'b11: mem_out = { 16'b0, mem[word_addr][31:16]};
    endcase
    default:      // lw      really 3010
                    mem_out = mem[word_addr];
    endcase
else
    mem_out = 32'd0;
end
`endif
endmodule

```

### Verilog file: address\_decoder.v

```
module AddressDecoder(
    input  [31:0] data_address,
    input          data_read_en,
    input          data_write_en,
    input  [31:0] data_write_value,
    input  [2:0]  data_size,

    output [31:0] mem_address,
    output          mem_read_en,
    output          mem_write_en,
    output [31:0] mem_write_value,
    output [2:0]  mem_data_size,

    output [31:0] io_address,
    output          io_read_en,
    output          io_write_en,
    output [31:0] io_write_value,
    output [2:0]  io_data_size,

    output          is_io
);

    wire          is_mem;

    assign io_address = data_address;
    assign mem_address = data_address;           // bit 31 is already 0

    // Is this a memory or IO address?
    assign is_mem = !data_address[31];          // bit 31 is 0
    assign is_io = data_address[31];           // bit 31 is 1

    // Memory and IO enable read and write flags
    assign mem_read_en = data_read_en && is_mem;
    assign mem_write_en = data_write_en && is_mem;
    assign io_read_en = data_read_en && is_io;
    assign io_write_en = data_write_en && is_io;

    assign mem_write_value = data_write_value;
```



### Verilog file: br\_comp.v

```
module BranchComp(  
    input [31:0] a,  
    input [31:0] b,  
    input [2:0] branch_cond,  
    output reg branch);  
  
always @(*)  
    case (branch_cond)  
        3'b000: branch = (a == b) ? 1 : 0;  
        3'b001: branch = (a != b) ? 1 : 0;  
        3'b110: branch = (a < b) ? 1 : 0;  
        3'b111: branch = (a >= b) ? 1 : 0;  
        3'b100: branch = ($signed(a) < $signed(b)) ? 1 : 0;  
        3'b101: branch = ($signed(a) >= $signed(b)) ? 1 : 0;  
        3'b010: branch = 0; // no branch  
        3'b011: branch = 1; // always branch  
        default: branch = 0; // no branch  
    endcase  
endmodule
```

## Verilog file: top.v

```
module ALU(  
    input  [31:0] a,           // source 1  
    input  [31:0] b,           // source 2  
    input  [3:0]  alu_control, // function select  
  
    output reg [31:0] result    //result  
);  
  
always @(*)  
    begin  
        case(alu_control)  
            4'b0000: result = a + b;           // add  
            4'b1000: result = a - b;           // sub  
            4'b0001: result = a << b[4:0];     // sll  
            4'b0010: result = $signed(a) < $signed(b) ? 32'd1 : 32'd0; // slt  
            4'b0011: result = a < b ? 32'd1 : 32'd0; // sltu  
            4'b0100: result = a ^ b;           // xor  
            4'b0101: result = a >> b[4:0];     // srl  
            4'b1101: result = a >>> b[4:0];    // sra  
            4'b0110: result = a | b;           // or  
            4'b0111: result = a & b;           // and  
            default: result = a + b;           // add  
        endcase  
    end  
endmodule
```

### Verilog file: reg\_file.v

```
module RegisterUnit(
    input      clk,
    input      reg_write_en,
    input  [4:0] rd,
    input  [31:0] rd_value,
    input  [4:0] rs1,
    input  [4:0] rs2,
    output [31:0] rs1_value,
    output [31:0] rs2_value
);

    reg  [31:0] reg_array [31:0];

    integer i;
    initial begin
        reg_array[0] = 32'hffff;           // set x0 to be hffff so if anything does
        read or write (bug) then we can tell
        for(i = 1; i <= 31; i = i + 1)
            reg_array[i] <= 32'd0;
        end

    always @ (posedge clk ) begin
        if (reg_write_en && (rd != 0)) begin
            reg_array[rd] <= rd_value;
        end
    end

    assign rs1_value = (rs1 == 0) ? 0 : reg_array[rs1];
    assign rs2_value = (rs2 == 0) ? 0 : reg_array[rs2];

endmodule
```

## Verilog file: mux.v

```
module Mux2_32(  
    input        sel,  
    output [31:0] out,  
    input [31:0] in0,    // chosen when sel == 0  
    input [31:0] in1    // chosen when sel == 1  
);  
  
    assign out = sel ? in1 : in0;  
endmodule  
  
module Mux4_32(  
    input        [1:0] sel,  
    output reg [31:0] out,  
    input [31:0] in0,    // chosen when sel == 0  
    input [31:0] in1,    // chosen when sel == 1  
    input [31:0] in2,    // chosen when sel == 2  
    input [31:0] in3    // chosen when sel == 3  
);  
  
    always @(*)  
        begin  
            case(sel)  
                2'b00: out = in0;  
                2'b01: out = in1;  
                2'b10: out = in2;  
                2'b11: out = in3;  
                default: out = in0;  
            endcase  
        end  
endmodule
```

# Testbench

## Verilog file: testbench.v

```
`timescale 1ns / 1ps

`include "settings.vh"

`define get_31_24(v)      ((v & 32'hff00_0000) >> 24)
`define get_23_16(v)      ((v & 32'h00ff_0000) >> 16)
`define get_15_8(v)        ((v & 32'h0000_ff00) >> 8)
`define get_7_0(v)         (v & 32'h0000_00ff)

`define make_word(v1, v2, v3,v4)    {v1, v2, v3, v4}
`define make_half(v1, v2)          {v1, v2}

`ifdef BANKED_MEM

`define memA(a)                uut.datapath.dm.memA[a>>2]
`define memB(a)                uut.datapath.dm.memB[a>>2]
`define memC(a)                uut.datapath.dm.memC[a>>2]
`define memD(a)                uut.datapath.dm.memD[a>>2]
`define set_memw(a, v)          `memD(a) <= `get_7_0(v); `memC(a) <= `get_15_8(v); `memB(a)
<= `get_23_16(v); `memA(a) <= `get_31_24(v)
`define show_memw(a)            $display("\tmemw{%1d}:   %8h", a, `make_word(`memA(a),
`memB(a), `memC(a), `memD(a)) )
`define check_memw(a, v, em, sm) if (`make_word(`memA(a), `memB(a), `memC(a), `memD(a))
!= v) $display(em); else $display(sm)

`else

`define memW(a)                uut.datapath.dm.mem[a>>2]
`define set_memw(a, v)          `memW(a) <= v
`define show_memw(a)            $display("\tmemw{%1d}:   %8h", a, `memW(a))
`define check_memw(a, v, em, sm) if (`memW(a) != v) begin $display(em); fails = fails +
1; end else $display(sm)

`endif

`define register(r)            uut.datapath.reg_file.reg_array[r]
`define set_reg(r, v)           uut.datapath.reg_file.reg_array[r] <= v
`define set_pc(a)               uut.datapath.pc_current <= a
`define set_instr(a, v)         uut.datapath.im.memory[a] <= v

`define show_state              $display("PC: %8h Instruction: %32b Opcode: %7b",
uut.datapath.pc_current, uut.datapath.instr, uut.datapath.opcode )

`define tick                    clk = ~clk; #5
`define clock_up                clk = 1; #5
`define clock_down              clk = 0; #5
`define run_step                `clock_down; `show_state; `clock_up

`define show_reg(r)             $display("\tx%1d:   %8h", r,
uut.datapath.reg_file.reg_array[r])
`define show_pcnext             $display("\tpc_next: %8h", uut.datapath.pc_next)
`define show_pc                 $display("\tpc: %8h", uut.datapath.pc_current)

`define check_pcnext(v, em, sm) if (uut.datapath.pc_next != v) begin $display(em);
fails = fails + 1; end else $display(sm)
`define check_pc(v, em, sm)     if (uut.datapath.pc_current != v) begin $display(em);
fails = fails + 1; end else $display(sm)
```

```

`define check_reg(r, v, em, sm) if (uut.datapath.reg_file.reg_array[r] != v) begin
$display(em); fails = fails + 1; end else $display(sm)

`define check_arith_reg(x1, x2, res, cmd, txt) `set_pc(0); \
`set_instr(0,
32'b00000000_00010_00001_000_00011_0110011 | (cmd << 12)); \
`set_reg(1, x1); \
`set_reg(2, x2); \
`run_step; \
`show_reg(3); \
if (`register(3) != res) begin
$display("%s %s", txt, "failed"); fails = fails + 1; end else $display("%s %s", txt,
"success")

module test_RISC32;

    // Inputs
    reg clk;

    // Instantiate the Unit Under Test (UUT)
    Risc32 uut (
        .clk(clk)
    );

    integer fails = 0;

    `ifdef PROG_BASIC
        initial
        begin
            clk <= 0;
            #200; // duration of the simulation
            $finish;
        end

        always
        begin
            #5 clk = ~clk;
        end

    `elsif PROG_STEPPED

        initial
        begin
            clk <= 0;
        end

        always
        begin
            #10;
            fails = 0;
            $display("RISC-V 32 bit - instruction memory: %4d data memory: %4d", `instr_bytes,
`data_bytes);

            `run_step;
            `show_reg(3);
            `check_reg(3, 32'h0001, "ldw fail", "ldw success");

            `run_step;
            `show_reg(1);
            `check_reg(1, 32'h0002, "ldw fail", "ldw success");

            `run_step;
            `show_reg(2);
            `check_reg(2, 32'h0003, "add fail", "add success");

            `run_step;

```

```

`show_memw(4);
`check_memw(4, 32'h0000_0003, "stw fail", "stw success");

`run_step;
`show_reg(2);
`check_reg(2, 32'hffff_ffff, "sub fail", "sub success");

`run_step;
`show_reg(2);
`check_reg(2, 32'hffff_ffff, "xori fail", "xori success");

`run_step;
`show_reg(2);
`check_reg(2, 32'h0000_0004, "sll fail", "sll success");

`run_step;
`show_reg(2);
`check_reg(2, 32'h0000_0000, "srl fail", "srl success");

`run_step;
`show_reg(2);
`check_reg(2, 32'h0000_0000, "and fail", "and success");

`run_step;
`show_reg(2);
`check_reg(2, 32'h0000_0003, "or fail", "or success");

`run_step;
`show_reg(2);
`check_reg(2, 32'h0000_0001, "slt fail", "slt success");

`run_step;
`show_reg(3);
`check_reg(3, 32'h0000_0002, "add fail", "add success");

`run_step;
`show_reg(3);
`check_reg(3, 32'h0000_1000, "lui fail", "lui success");

`run_step;
`show_reg(3);
`check_reg(3, 32'h0000_1034, "auipc fail", "auipc success");

`run_step;
`show_pc;
`check_pc(32'h0000_003c, "beq fail", "beq success");

`run_step;
`show_pc;
`check_pc(32'h0000_0044, "bne fail", "bne success");

`run_step;
`show_pc;
`check_pc(32'h0000_0010, "jalr fail - jump", "jalr success - jump");
`show_reg(1);
`check_reg(1, 32'h0000_0048, "jalr fail - store return address", "jalr success -
store return address");

// can check it like this
//`clock_down;
//`show_state;
//`show_pcnext;
//`check_pcnext(32'h0000_0010, "jalr fail - jump");
//`clock_up;
//`show_reg(1);
//`check_reg(1, 32'h0000_0048, "jalr fail - store return address");

```

```

        $display("Testbench complete: %d fails", fails);
        #20;
        $finish;
    end

`elsif PROG_INDIV
    initial
        begin
            clk <=0;
        end

    always
        begin
            #10;
            fails = 0;
            $display("RISC-V 32 bit - instruction memory: %4d data memory: %4d",
`instr_bytes, `data_bytes);

            `check_arith_reg(1, 5, 6, 3'b000, "add");
            `check_arith_reg(32'hffff_ffff, 5, 4, 3'b000, "add");
            `check_arith_reg(3, 4, 7, 3'b110, "or");
            `check_arith_reg(32'h55, 32'h50, 32'h5, 3'b100, "xor");
            `check_arith_reg(32'h55, 32'h55, 32'h0, 3'b100, "xor");
            `check_arith_reg(32'h55, 32'h50, 32'h50, 3'b111, "and");

            // Test lw x1, [0 + x2]
            // Objective - show that a memory word load works
            //          lw rd, rs1(ext_imm)
            //          +++imm+++++_rs1+_010_++rd+_++op+++
            `set_pc(0);
            `set_instr(0, 32'b000000000000_00010_010_00001_0000011);
            `set_memw(4, 32'h0000_7f7f);
            `set_reg(2, 32'h0004); // x2 = 4
            `run_step;
            `show_reg(1);
            `check_reg(1, 32'h0000_7f7f, "lw failure", "lw success");

            // Test add x3, x1, x2
            // Objective - show that add of hfff and 1 is h1000
            //          add rd, rs1, rs2
            //          +func7+_rs2+_rs1+_fu3_++rd+_+++op++
            `set_pc(0);
            `set_instr(0, 32'b00000000_00010_00001_000_00011_0110011);
            `set_reg(1, 32'h0001);
            `set_reg(2, 32'h0fff);
            `set_reg(3, 32'h2222);
            `run_step;
            `show_reg(3);
            `check_reg(3, 32'h0000_1000, "add failure", "add success");

            // Test lui x1, h55555
            // Objective - show that lui loads the upper 20 bits
            //          lui rd, imm
            //          ++++++imm+++++_++rd+_+++op++
            `set_pc(0);
            `set_instr(0, 32'b010101010101010101_00001_0110111);
            `set_reg(1, 32'h0000_0000);
            `run_step;
            `show_reg(1);
            `check_reg(1, 32'h5555_5000, "lui failure", "lui success");

            // Test memory wrap - lw x1, x2(0) (128) should wrap to 0
            // Objective - show that accessing the word *above* the last word in memory wraps
to 0
            //          lw rd, rs1(ext_imm)

```



```

//          +++imm+++++_rs1+_xxx_++rd_++op+++
`set_pc(0);
`set_instr(0, 32'b000000000000_00010_010_00001_0000011);
`set_memw(0, 32'h7f7f_f7f7);
`set_memw(124, 32'h8888_8888);
`set_reg(2, 32'd128);
`run_step;
`show_reg(1);
`check_reg(1, 32'h7f7f_f7f7, "lw memory wrap failure", "lw memory wrap
success");

// Test memory top - lw x1, x2(0)    (124)
// Objective - show that a read from last word in memory works
//          lw rd, rs1(ext_imm)
//          +++imm+++++_rs1+_010_++rd_++op+++
`set_pc(0);
`set_instr(0, 32'b000000000000_00010_010_00001_0000011);
`set_memw(0, 32'h7f7f_f7f7);
`set_memw(124, 32'h8888_8888);
`set_reg(2, 32'd124);
`run_step;
`show_reg(1);
`check_reg(1, 32'h8888_8888, "lw memory top failure", "lw memory top success");

// Test lh x1, [0 + x2]
// Objective - show lh does not retrieve the higher two bytes but sets to zero
//          lh rd, rs1(ext_imm)
//          +++imm+++++_rs1+_001_++rd_++op+++
`set_pc(0);
`set_instr(0, 32'b000000000000_00010_001_00001_0000011);
`set_memw(0, 32'h7f7f_f7f7);
`set_reg(2, 32'h0004);
`run_step;
`show_reg(1);
`check_reg(1, 32'h0000_7f7f, "lh failure", "lh success");

// Test lb x1, [0 + x2]
// Objective - show lb does not sign extend when top bit is 0 (ok, it does - but
sign extends 0)
//          lb rd, rs1(ext_imm)
//          +++imm+++++_rs1+_000_++rd_++op+++
`set_pc(0);
`set_instr(0, 32'b000000000000_00010_000_00001_0000011);
`set_memw(0, 32'h7f7f_7f7f);
`set_reg(2, 32'h0004);
`run_step;
`show_reg(1);
`check_reg(1, 32'h0000_007f, "lb (7f) failure", "lb (7f) success");

// Test lb x1, [0 + x2]
// Objective - show lb does sign extend when top bit is 1
//          lb rd, rs1(ext_imm)
//          +++imm+++++_rs1+_000_++rd_++op+++
`set_pc(0);
`set_instr(0, 32'b000000000000_00010_000_00001_0000011);
`set_memw(4, 32'h7777_778f);
`set_reg(2, 32'h0004);
`run_step;
`show_reg(1);
`check_reg(1, 32'hffff_ff8f, "lb (8f) failure", "lb (8f) success");

// Test lhu x1, [0 + x2]
// Objective - show lhu does not sign extend the half-word on load
//          lhu rd, rs1(ext_imm)
//          +++imm+++++_rs1+_101_++rd_++op+++
`set_pc(0);

```

```

`set_instr(0, 32'b000000000000_00010_101_00001_0000011);
`set_memw(4, 32'h7777_8f8f);
`set_reg(2, 32'h0004);
`run_step;
`show_reg(1);
`check_reg(1, 32'h0000_8f8f, "lhu failure", "lhu success");

// Test sh x1, [0 + x2]
// Objective - show sh only updates lower two bytes in memory
//             sh rs2, rs1(ext_imm)
//             +++imm+_rs2+_rs1+_001_+imm+_+op+++
`set_pc(0);
`set_instr(0, 32'b00000000_00001_00010_001_00000_0100011);
`set_memw(4, 32'h7777_8f8f);
`set_reg(2, 32'h0004);
`set_reg(1, 32'h9999_9999);
`run_step;
`show_memw(4);
`check_memw(4, 32'h7777_9999, "sh failure", "sh success");

$display("Testbench complete: %d fails", fails);
#20;
$finish;
end
`endif
endmodule

```

## Another heading

Xxxx

Xxxx

Xxxx

# Instruction Set Architecture

instruction	imm	opcode	fun3	fun7	operation
lui rd, imm20	U	0x37			rd = imm20 << 12
auipc rd, imm20	U	0x17			rd = pc + (imm20 <<12)
addi rd, rs1, imm12	I	0x13	000		rd = rs1 + se(imm12)
slli rd, rs1, imm12	I	0x13	001	0x00	rd = rs1 << imm12[4:0]
slti rd, rs1, imm12	I	0x13	010		rd = rs1 < signed se(imm12) ? 1 : 0
sltiu rd, rs1, imm12	I	0x13	011		rd = rs1 < unsign se(imm12) ? 1 : 0
xori rd, rs1, imm12	I	0x13	100		rd = rs1 ^ se(imm12)
srli rd, rs1, imm12	I	0x13	101	0x00	rd = rs1 >> imm12[4:0]
srai rd, rs1, imm12	I	0x13	101	0x20	rd = rs1 >>> imm12[4:0]
ori rd, rs1, imm12	I	0x13	110		rd = rs1   se(imm12)
andi rd, rs1, imm12	I	0x13	111		rd = rs1 & se(imm12)
add rd, rs1, rs2	R	0x33	000	0x00	rd = rs1 + rs2
sub rd, rs1, rs2	R	0x33	000	0x20	rd = rs1 - rs2
sll rd, rs1, rs2	R	0x33	001		rd = rs1 << rs2[4:0]
slt rd, rs1, rs2	R	0x33	010		rd = rs1 < signed rs2 ? 1 : 0
sltu rd, rs1, rs2	R	0x33	011		rd = rs1 < unsign rs2 ? 1 : 0
xor rd, rs1, rs2	R	0x33	100		rd = rs1 ^ rs2
srl rd, rs1, rs2	R	0x33	101	0x00	rd = rs1 >> rs2[4:0]
sra rd, rs1, rs2	R	0x33	101	0x20	rd = rs1 >>> rs2[4:0]
or rd, rs1, rs2	R	0x33	110		rd = rs1   rs2
and rd, rs1, rs2	R	0x33	111		rd = rs1 & rs2
lb rd, imm12(rs1)	I	0x03	000		rd = se(mem[rs1 + se(imm12)][7:0])
lh rd, imm12(rs1)	I	0x03	001		rd = se(mem[rs1 + se(imm12)][15:0])
lw rd, imm12(rs1)	I	0x03	010		rd = mem[rs1 + se(imm12)][31:0]
lbu rd, imm12(rs1)	I	0x03	100		rd = ze(mem[rs1 + se(imm12)][7:0])
lhu rd, imm12(rs1)	I	0x03	101		rd = ze(mem[rs1 + se(imm12)][15:0])
sb rs2, imm12(rs1)	S	0x23	000		mem[rs1 + se(imm12)][7:0] = rs2[7:0]
sh rs2, imm12(rs1)	S	0x23	001		mem[rs1 + se(imm12)][15:0] = rs2[15:0]
sw rs2, imm12(rs1)	S	0x23	010		mem[rs1 + se(imm12)][31:0] = rs2
jal rd, targ20	J	0x6f			rd = pc+4; pc += se(targ20 <<1)
jalr rd, imm12(rs1)	I	0x67	000		rd = pc+4; pc = (rs1 + se(imm12)) & ~1
beq rs1, rs2, targ12	B	0x63	000		if (rs1 == rs2) pc += se(targ12<<1)
bne rs1, rs2, targ12	B	0x63	001		if (rs1 != rs2) pc += se(targ12<<1)
blt rs1, rs2, targ12	B	0x63	100		if (rs1 < signed rs2) pc += se(targ12<<1)
bge rs1, rs2, targ12	B	0x63	101		if (rs1 >= signed rs2) pc += se(targ12<<1)
bltu rs1, rs2, targ12	B	0x63	110		if (rs1 < unsign rs2) pc += se(targ12<<1)
bgeu rs1, rs2, targ12	B	0x63	111		if (rs1 >= unsign rs2) pc += se(targ12<<1)

In this implementation all half-word accesses must be half-word aligned, this is enforced by removing the lowest bit of the memory address


Also all word accesses must be word aligned, this is enforced by removing the lowest two bits of the memory address

instruction	imm	opcode	fun3	fun7	operation
lh rd, imm12(rs1)	I	0x03	001		rd = se((mem[rs1 + se(imm12)] & ~1)[15:0])
lhu rd, imm12(rs1)	I	0x03	101		rd = ze((mem[rs1 + se(imm12)] & ~1)[15:0])
sh rs2, imm12(rs1)	S	0x23	001		mem[(rs1 + se(imm12)) & ~1][15:0] = rs2[15:0]
lw rd, imm12(rs1)	I	0x03	010		rd = mem[(rs1 + se(imm12)) & ~3][31:0]
sw rs2, imm12(rs1)	S	0x23	010		mem[(rs1 + se(imm12)) & ~3][31:0] = rs2

instruction	imm	opcode	fun3	fun7	encoding
lui rd, imm20	U	0x37			iiii iiii iiii iiii iiii dddd d011 0111
auipc rd, imm20	U	0x17			iiii iiii iiii iiii iiii dddd d001 0111
addi rd, rs1, imm12	I	0x13	000		iiii iiii iiii ssss s000 dddd d001 0011
slli rd, rs1, imm12	I	0x13	001	0x00	0000 000i iiii ssss s001 dddd d001 0011
slti rd, rs1, imm12	I	0x13	010		iiii iiii iiii ssss s010 dddd d001 0011
sltiu rd, rs1, imm12	I	0x13	011		iiii iiii iiii ssss s011 dddd d001 0011
xori rd, rs1, imm12	I	0x13	100		iiii iiii iiii ssss s100 dddd d001 0011
srlr rd, rs1, imm12	I	0x13	101	0x00	0000 000i iiii ssss s101 dddd d001 0011
srair rd, rs1, imm12	I	0x13	101	0x20	0100 000i iiii ssss s101 dddd d001 0011
ori rd, rs1, imm12	I	0x13	110		iiii iiii iiii ssss s110 dddd d001 0011
andi rd, rs1, imm12	I	0x13	111		iiii iiii iiii ssss s111 dddd d001 0011
add rd, rs1, rs2	R	0x33	000	0x00	0000 000t tttt ssss s000 dddd d011 0011
sub rd, rs1, rs2	R	0x33	000	0x20	0100 000t tttt ssss s000 dddd d011 0011
sll rd, rs1, rs2	R	0x33	001		0000 000t tttt ssss s001 dddd d011 0011
slt rd, rs1, rs2	R	0x33	010		0000 000t tttt ssss s010 dddd d011 0011
sltu rd, rs1, rs2	R	0x33	011		0000 000t tttt ssss s011 dddd d011 0011
xor rd, rs1, rs2	R	0x33	100		0000 000t tttt ssss s100 dddd d011 0011
srl rd, rs1, rs2	R	0x33	101	0x00	0000 000t tttt ssss s101 dddd d011 0011
sra rd, rs1, rs2	R	0x33	101	0x20	0100 000t tttt ssss s101 dddd d011 0011
or rd, rs1, rs2	R	0x33	110		0000 000t tttt ssss s110 dddd d011 0011
and rd, rs1, rs2	R	0x33	111		0000 000t tttt ssss s111 dddd d011 0011
lb rd, imm12(rs1)	I	0x03	000		iiii iiii iiii ssss s000 dddd d000 0011
lh rd, imm12(rs1)	I	0x03	001		iiii iiii iiii ssss s001 dddd d000 0011
lw rd, imm12(rs1)	I	0x03	010		iiii iiii iiii ssss s010 dddd d000 0011
lbu rd, imm12(rs1)	I	0x03	100		iiii iiii iiii ssss s100 dddd d000 0011
lhu rd, imm12(rs1)	I	0x03	101		iiii iiii iiii ssss s101 dddd d000 0011
sb rs2, imm12(rs1)	S	0x23	000		iiii iiit tttt ssss s000 dddd d010 0011
sh rs2, imm12(rs1)	S	0x23	001		iiii iiit tttt ssss s001 dddd d010 0011
sw rs2, imm12(rs1)	S	0x23	010		iiii iiit tttt ssss s010 dddd d010 0011
jal rd, targ20	J	0x6f			iiii iiii iiii iiii iiii dddd d110 0111
jalr rd, imm12(rs1)	I	0x67	000		iiii iiii iiii ssss s000 dddd d110 0111
beq rs1, rs2, targ12	B	0x63	000		iiii iiit tttt ssss s000 dddd d110 0011
bne rs1, rs2, targ12	B	0x63	001		iiii iiit tttt ssss s001 dddd d110 0011
blt rs1, rs2, targ12	B	0x63	100		iiii iiit tttt ssss s100 dddd d110 0011
bge rs1, rs2, targ12	B	0x63	101		iiii iiit tttt ssss s101 dddd d110 0011
bltu rs1, rs2, targ12	B	0x63	110		iiii iiit tttt ssss s110 dddd d110 0011
bgeu rs1, rs2, targ12	B	0x63	111		iiii iiit tttt ssss s111 dddd d110 0011

instruction	imm	opcode	fun3	fun7	operation	encoding
lui rd, imm20	U	0x37			rd = imm20 << 12	iiii iiii iiii iiii iiii iiii dddd d011 0111
auipc rd, imm20	U	0x17			rd = pc + (imm20 <<12)	iiii iiii iiii iiii iiii iiii dddd d001 0111
addi rd, rs1, imm12	I	0x13	000		rd = rs1 + se(imm12)	iiii iiii iiii iiii ssss s000 dddd d001 0011
slli rd, rs1, imm12	I	0x13	001	0x00	rd = rs1 << imm12[4:0]	0000 000i iiii ssss s001 dddd d001 0011
slti rd, rs1, imm12	I	0x13	010		rd = rs1 < signed se(imm12) ? 1 : 0	iiii iiii iiii iiii ssss s010 dddd d001 0011
sltiu rd, rs1, imm12	I	0x13	011		rd = rs1 < unsign se(imm12) ? 1 : 0	iiii iiii iiii iiii ssss s011 dddd d001 0011
xori rd, rs1, imm12	I	0x13	100		rd = rs1 ^ se(imm12)	iiii iiii iiii iiii ssss s100 dddd d001 0011
srlw rd, rs1, imm12	I	0x13	101	0x00	rd = rs1 >> imm12[4:0]	0000 000i iiii ssss s101 dddd d001 0011
sraiw rd, rs1, imm12	I	0x13	101	0x20	rd = rs1 >>> imm12[4:0]	0100 000i iiii ssss s101 dddd d001 0011
ori rd, rs1, imm12	I	0x13	110		rd = rs1   se(imm12)	iiii iiii iiii iiii ssss s110 dddd d001 0011
andi rd, rs1, imm12	I	0x13	111		rd = rs1 & se(imm12)	iiii iiii iiii iiii ssss s111 dddd d001 0011
add rd, rs1, rs2	R	0x33	000	0x00	rd = rs1 + rs2	0000 000t tttt ssss s000 dddd d011 0011
sub rd, rs1, rs2	R	0x33	000	0x20	rd = rs1 - rs2	0100 000t tttt ssss s000 dddd d011 0011
sll rd, rs1, rs2	R	0x33	001		rd = rs1 << rs2[4:0]	0000 000t tttt ssss s001 dddd d011 0011
slt rd, rs1, rs2	R	0x33	010		rd = rs1 < signed rs2 ? 1 : 0	0000 000t tttt ssss s010 dddd d011 0011
sltu rd, rs1, rs2	R	0x33	011		rd = rs1 < unsign rs2 ? 1 : 0	0000 000t tttt ssss s011 dddd d011 0011
xor rd, rs1, rs2	R	0x33	100		rd = rs1 ^ rs2	0000 000t tttt ssss s100 dddd d011 0011
srl rd, rs1, rs2	R	0x33	101	0x00	rd = rs1 >> rs2[4:0]	0000 000t tttt ssss s101 dddd d011 0011
sra rd, rs1, rs2	R	0x33	101	0x20	rd = rs1 >>> rs2[4:0]	0100 000t tttt ssss s101 dddd d011 0011
or rd, rs1, rs2	R	0x33	110		rd = rs1   rs2	0000 000t tttt ssss s110 dddd d011 0011
and rd, rs1, rs2	R	0x33	111		rd = rs1 & rs2	0000 000t tttt ssss s111 dddd d011 0011
lb rd, imm12(rs1)	I	0x03	000		rd = se(mem[rs1 + se(imm12)][7:0])	iiii iiii iiii iiii ssss s000 dddd d000 0011
lh rd, imm12(rs1)	I	0x03	001		rd = se(mem[rs1 + se(imm12)][15:0])	iiii iiii iiii iiii ssss s001 dddd d000 0011
lw rd, imm12(rs1)	I	0x03	010		rd = mem[rs1 + se(imm12)][31:0]	iiii iiii iiii iiii ssss s010 dddd d000 0011
lbu rd, imm12(rs1)	I	0x03	100		rd = ze(mem[rs1 + se(imm12)][7:0])	iiii iiii iiii iiii ssss s100 dddd d000 0011
lhu rd, imm12(rs1)	I	0x03	101		rd = ze(mem[rs1 + se(imm12)][15:0])	iiii iiii iiii iiii ssss s101 dddd d000 0011
sb rs2, imm12(rs1)	S	0x23	000		mem[rs1 + se(imm12)][7:0] = rs2[7:0]	iiii iiii tttt ssss s000 dddd d010 0011
sh rs2, imm12(rs1)	S	0x23	001		mem[rs1 + se(imm12)][15:0] = rs2[15:0]	iiii iiii tttt ssss s001 dddd d010 0011
sw rs2, imm12(rs1)	S	0x23	010		mem[rs1 + se(imm12)][31:0] = rs2	iiii iiii tttt ssss s010 dddd d010 0011
jal rd, targ20	J	0x6f			rd = pc+4; pc += se(targ20 <<1)	iiii iiii iiii iiii iiii iiii dddd d110 0111
jalr rd, imm12(rs1)	I	0x67	000		rd = pc+4; pc = (rs1 + se(imm12)) & ~0x1	iiii iiii iiii iiii ssss s000 dddd d110 0111
beq rs1, rs2, targ12	B	0x63	000		if (rs1 == rs2) pc += se(targ12<<1)	iiii iiii tttt ssss s000 dddd d110 0011
bne rs1, rs2, targ12	B	0x63	001		if (rs1 != rs2) pc += se(targ12<<1)	iiii iiii tttt ssss s001 dddd d110 0011
blt rs1, rs2, targ12	B	0x63	100		if (rs1 < signed rs2) pc += se(targ12<<1)	iiii iiii tttt ssss s100 dddd d110 0011
bge rs1, rs2, targ12	B	0x63	101		if (rs1 >= signed rs2) pc += se(targ12<<1)	iiii iiii tttt ssss s101 dddd d110 0011
bltu rs1, rs2, targ12	B	0x63	110		if (rs1 < unsign rs2) pc += se(targ12<<1)	iiii iiii tttt ssss s110 dddd d110 0011
bgeu rs1, rs2, targ12	B	0x63	111		if (rs1 >= unsign rs2) pc += se(targ12<<1)	iiii iiii tttt ssss s111 dddd d110 0011

	31	30	29	28	27	26	25	24	23	22	21	20	19	18	17	16	15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0				
Load	I	imm[11:0]											rs1			funct3			rd			op														
Store	S	imm[11:5]					rs2											rs1			funct3			imm[4:0]						op						
Data	R	funct7					rs2											rs1			funct3			rd			op									
Load imm	U	imm[31:12]											rd															op								
Branch	B	i[12]	imm[10:5]					rs2											rs1			funct3			imm[4:1]			i[11]			op					
Jump	J	i[20]	imm[10:1]										i[11]			imm[19:12]											rd			op						
	31	30	29	28	27	26	25	24	23	22	21	20	19	18	17	16	15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0				
Load	I	inst[31]											inst[30:25]			inst[24:21]			i[20]																	
Store	S	inst[31]											inst[30:25]			inst[1:8]			i[7]																	
Load imm	U	i[31]					inst[30:20]										inst[19:12]											0								
Branch	B	inst[31]											i[7]			inst[30:25]			inst[1:8]			0														
Jump	J	inst[31]					imm[19:12]											i[20]			inst[30:25]			inst[24:21]						0						

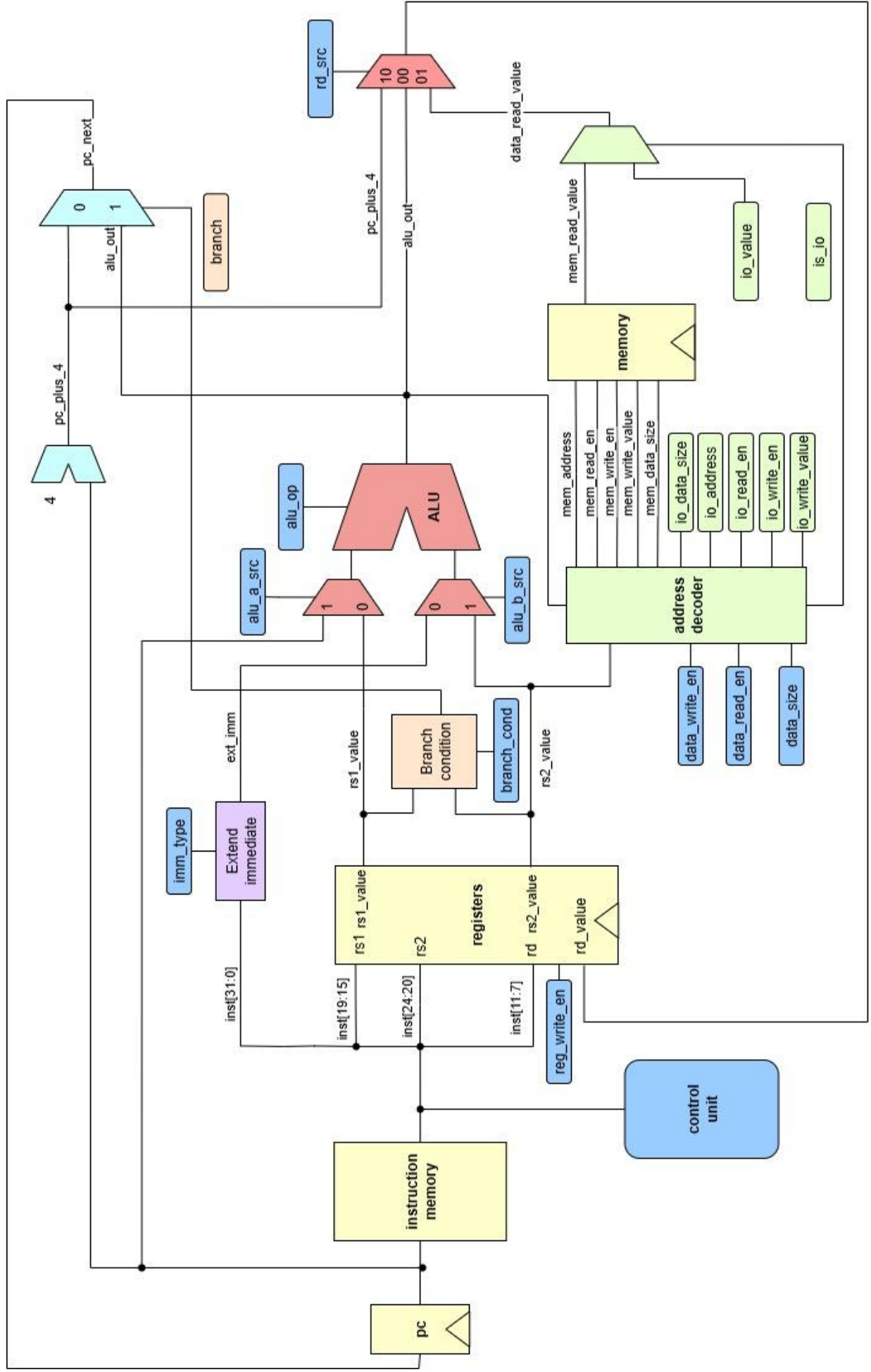




## References

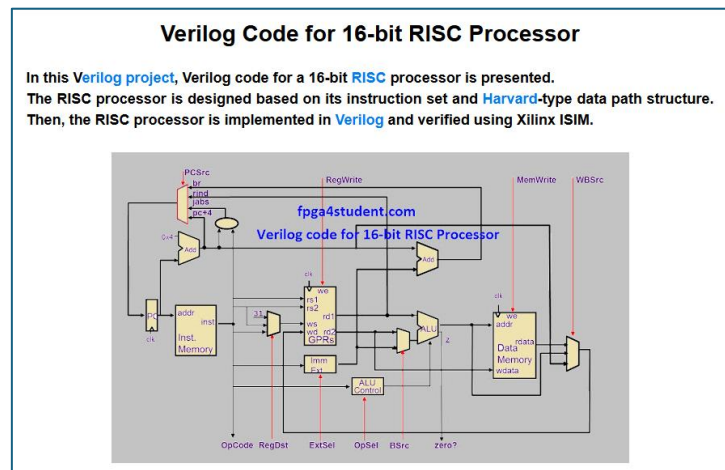
### fpga4student RISC processor design

<https://www.fpga4student.com/2017/04/verilog-code-for-16-bit-risc-processor.html>



### Digital Design and Computer Architecture – RISC V Edition

ISBN: 978-0-12-820064-3

 

### ISA documentation

<https://www.five-embeddev.com/riscv-user-isa-manual/latest-adoc/>